

EXP 7: Current-mode biquad using a current conveyor (CC II+)

(Lab Report by Sanuj Kulshrestha, 2017UEC2053, ECD07, Semester 6)

AIM:

1. Verify that the circuit shown in Figure 2 realizes a low pass, bandpass and high pass filter as follows:
 - a. Low pass: $i_1 = i_3 = 0$, $i_2 = i_{in}$
 - b. Band pass: $i_1 = i_2 = 0$, $i_3 = i_{in}$
 - c. High pass: $i_1 = -i_2$ and $i_3 = i_1(R_1/R_2)(1 + C_2/C_1)$
2. Discuss Limitations of the circuit
3. Comment upon if this is the only single CCII/single CFOA circuit which can realise an Universal filter?
4. Find out by searching the literature if there is any similar circuit known which can realise universal filter using a single CCII/CFOA in voltage mode i.e inputs and output both being voltages rather than currents?

Ckt Analysis

- $V_{out} = -i_z R_L$ — (1)
- $i_z - I_1 = \frac{e_2 - e_1}{R_1}$ — (2)
- $I_3 = -(e_1 - e_2) sC_2 + \frac{e_1}{R_2}$ — (3)
- $= -sC_2 R_1 (i_z - I_1) + \frac{e_1}{R_2}$
- $\Rightarrow e_1 = R_2 I_3 + sC_2 R_1 (i_z - I_1) R_2$ — (4)
- and
- $e_2 = R_1 (i_z - I_1) + e_1$
- $= (R_1 + sC_2 R_1 R_2) i_z - (R_1 + sC_2 R_1 R_2) I_1 + R_2 I_3$ — (5)
- $I_2 + (e_1 - e_2) sC_2 = i_z - I_1 + e_2 sC_2$
- Substituting e_2 from (5) & (2)
- $\Rightarrow I_2 + -sC_2 R_1 (i_z - I_1) = i_z - I_1 + sC_2 [(R_1 + sC_2 R_1 R_2)(i_z - I_1) + R_2 I_3]$
- $\Rightarrow I_1 [sC_2 R_1 + sC_2 R_1 + s^2 C_2^2 R_1 R_2 + 1] - I_3 [sC_2 R_2] + I_2 = i_z [sC_2 R_1 + sC_2 R_1 + s^2 C_2^2 R_1 R_2 + 1]$
- $\Rightarrow \boxed{i_z = I_1 + \frac{I_2}{D(s)} - \frac{I_3 sC_2 R_2}{D(s)}}$
- where $D(s) = s^2 C_2^2 R_1 R_2 + s[C_2 R_1 + C_2 R_1] + 1$

1. SPICE ANALYSIS

a. LOW PASS


```
.include /Users/sanujku/Documents/LTspice/libraries/ad844.cir
*Xn Y X +V -V W Z MODELNAME
X1 3 2 7 4 6 5 AD844

R1 2 1 1k
R2 3 0 500
RL 0 5 10k

C1 1 0 1n
C2 1 3 1n


I1 0 8 AC 0m
I2 0 1 AC 1m
I3 0 3 AC 0m
*For HIGH PASS I3 needs to be  $i1(R1/R2)(1 + C2/C1) = 4*I1$ 
*F3 0 3 VI1 4
*0V voltage source for current dependent(I1) current source(I3)
VI1 8 2 DC 0V
VccPositive 7 0 DC 12V
VccNegative 4 0 DC -12V

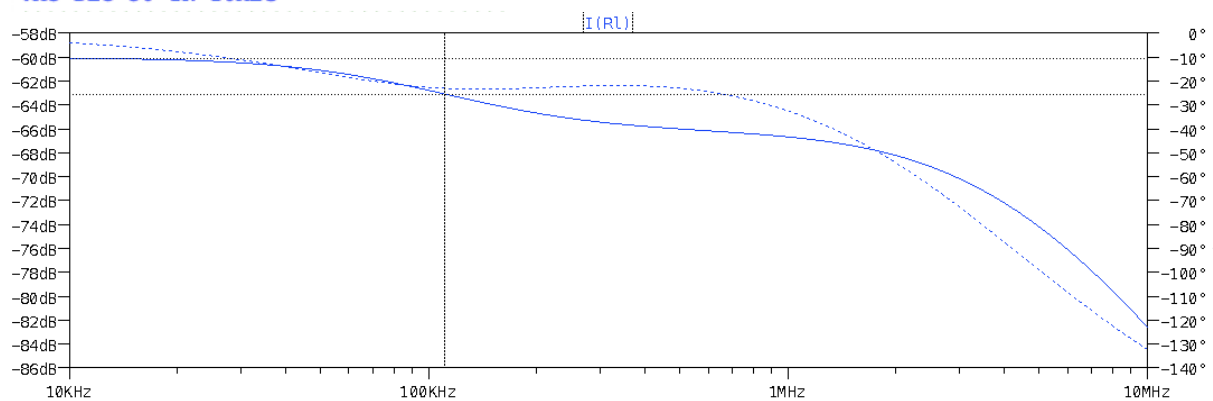***** OUTPUT CODES *****
*AC ANALYSIS
.AC DEC 50 1K 10MEG
```



Observation:

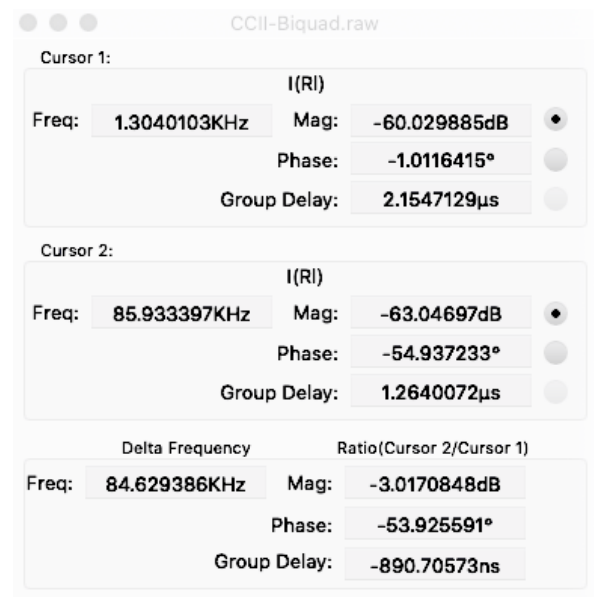1. At DC, Mag = -60.08 dB
2. At freq = 111 KHz, Mag = -63.08dB
3. Therefore, 3 db BW = 111 KHz
4. At 225 KHz, Magnitude is equal to -64dB, hence there is drop of 4dB from that of voltage at DC.



b. BAND PASS

```
.include /Users/sanujkul/Documents/LTspice/libraries/ad844.cir
```

```
*Xn Y X +V -V W Z MODELNAME
```

```
X1 3 2 7 4 6 5 AD844
```

```
R1 2 1 1k
```

```
R2 3 0 500
```

```
RL 0 5 10k
```

```
C1 1 0 1n
```

```
C2 1 3 1n
```

```
I1 0 8 AC 0m
```

```
I2 0 1 AC 0m
```

```
I3 0 3 AC 1m
```

```
*For HIGH PASS I3 needs to be  $i1(R1/R2)(1 + C2/C1) = 4*I1$ 
```

```
*F3 0 3 VI1 4
```

```
*0V voltage source for current dependent(I1) current source(I3)
```

```
VI1 8 2 DC 0V
```


```
VccPositive 7 0 DC 12V
```

```
VccNegative 4 0 DC -12V
```

```
***** OUTPUT CODES *****
```

```
*AC ANALYSIS
```

```
.AC DEC 50 1K 10MEG
```

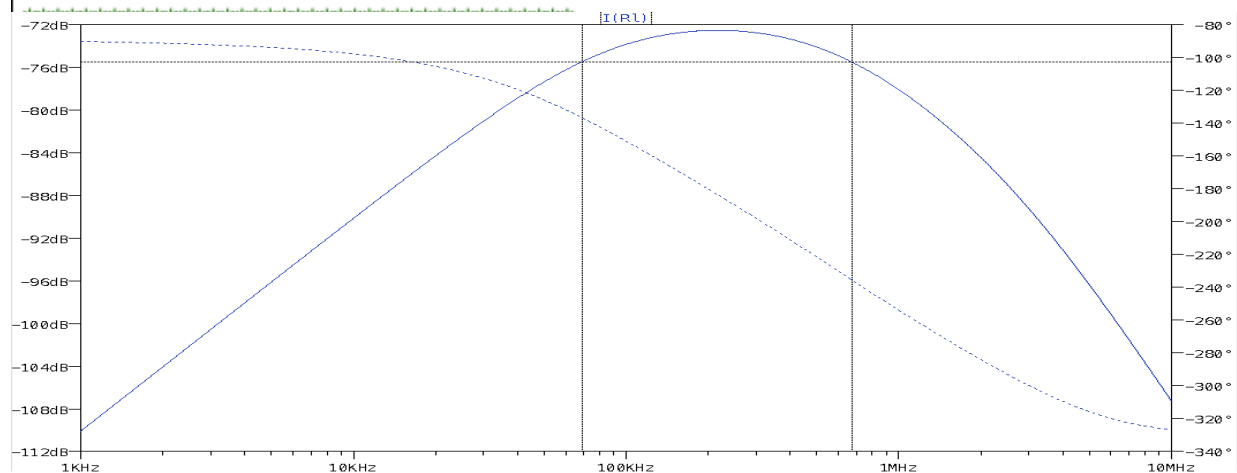

Observations:

1. Centre frequency = 217 kHz
2. Left -3dB freq = 68 kHz
3. Right -3db freq = 68 kHz
4. BW = 603 kHz

Cursor 1:			
I(R1)			
Freq:	672.00787KHz	Mag:	-75.465946dB
		Phase:	-235.39705°
		Group Delay:	194.71401ns
Cursor 2:			
I(R1)			
Freq:	68.761KHz	Mag:	-75.466332dB
		Phase:	-136.41702°
		Group Delay:	1.4603406µs
Delta Frequency		Ratio(Cursor 2/Cursor 1)	
Freq:	-603.24687KHz	Mag:	-386.58463µdB
		Phase:	98.980032°
		Group Delay:	1.2656265µs

c. HIGH PASS


```
.include /Users/sanujkul/Documents/LTspice/libraries/ad844.cir
*Xn Y X +V -V W Z MODELNAME
X1 3 2 7 4 6 5 AD844

R1 2 1 1k
R2 3 0 500
RL 0 5 10k

C1 1 0 1n
C2 1 3 1n


I1 0 8 AC 1m
I2 0 1 AC -1m
*I3 0 3 AC 1m
*For HIGH PASS I3 needs to be  $i1(R1/R2)(1 + C2/C1) = 4*I1$ 
F3 0 3 VI1 4
*0V voltage source for current dependent(I1) current source(I3)
VI1 8 2 DC 0V
VccPositive 7 0 DC 12V
VccNegative 4 0 DC -12V

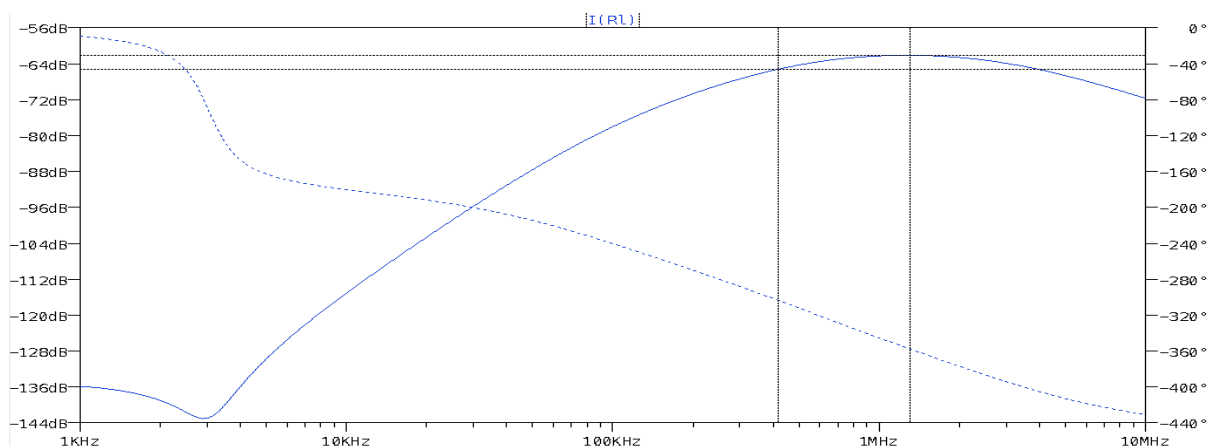***** OUTPUT CODES *****
*AC ANALYSIS
.AC DEC 50 1K 10MEG
```



Observations:

1. 3dB cutoff frequency = 420 KHz

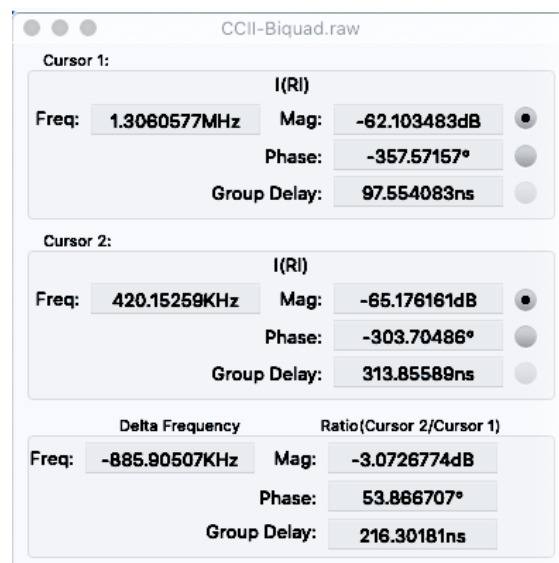

Limitations of the circuit:

1. For High pass response, there is too much dependencies among current sources.
2. Not adjustable filter parameters.
3. No feedback.

Comment upon if this is the only single CCII/single CFOA circuit which can realise an Universal filter?

No this is not the only single CCII/single CFOA based Universal filters. Some of other examples can be found in:

1. SUN, Y .-CH., HE, Y .-G. (2003) Active filters using single current conveyor.
2. Sharma, R. K., & Senani, R. (2004). *Universal current mode biquad using a single CFOA. International Journal of Electronics.*
3. Sharma, R. K., & Senani, R. (2004). *On the Realization of Universal Current Mode Biquads Using a Single CFOA. Analog Integrated Circuits and Signal Processing.*
(This paper has 8 Current mode universal filters using single CFOA)

Find out by searching the literature if there is any similar circuit known which can realise universal filter using a single CCII/CFOA in voltage mode i.e inputs and output both being voltages rather than currents?

1. Kaçar, F., & Yeşil, A. (2009). *Voltage mode universal filters employing single FDCCII. Analog Integrated Circuits and Signal Processing.*
(This paper has 4 Voltage mode universal biquads using single Fully Differential CCII)
2. Chen, H.-P. (2009). *Single CCII-based voltage-mode universal filter. Analog Integrated Circuits and Signal Processing*